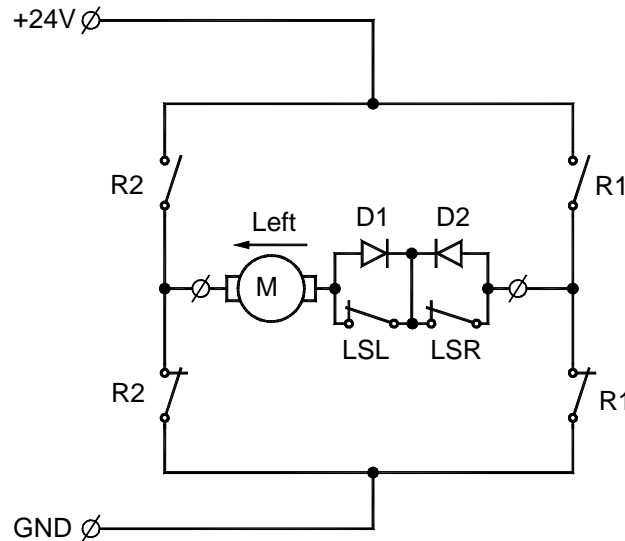


Fig. 2.13 The power circuit diagram for a direct on line starter

2. Make the required wiring and connections for the power circuit as shown in figure 2.14.



3. Once you are finished with the connections, call the instructor to check it for you and make sure that it is correct.